# **Project Proposal: Alarm System with Password Entry**

## **Project Overview:**

The Alarm System with Password Entry is a security system designed to provide protection against unauthorized access. The system requires users to enter a password using a 4x4 matrix keypad connected to an Artix A7 FPGA. If the entered password matches the predefined password, the system remains disarmed. However, an incorrect password triggers an alarm and activates a buzzer to indicate a security breach.

## **Components:**

- Artix A7 FPGA board
- 4x4 matrix keypad
- 3.Comparator
- SRLATCH
- Display (optional) for feedback messages
- Buzzer or alarm sound output

## **REQUIREMENT FOR OUR SYSTEM**

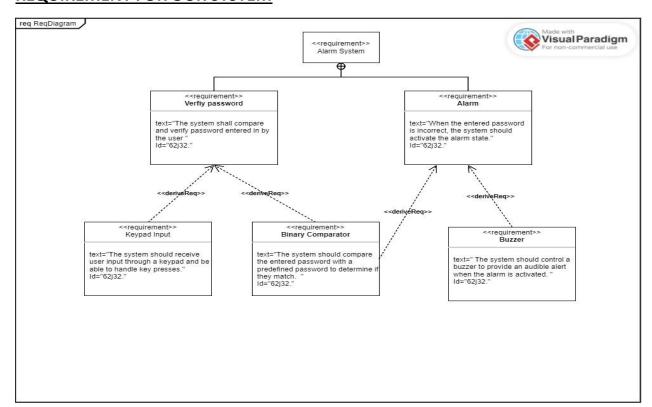


Figure 1 Requirement alarm system

## **BLOCK DIAGRAM**

	BINARY COMPARATOR (Keypad input =set password )	Made with Visual Paradigm For non-commercial use
Keypad 4x4Matrix (Input)		BUZZER
	SR-LATCH	

Figure 2 Block Diagram

## **Functionalities**

#### User Interface:

- The 4x4 matrix keypad allows users to enter the password.
- Optional display provides feedback messages, such as "Enter Password" or "Incorrect Password."

#### Password Entry:

- The FPGA scans the keypad to detect keypresses and converts them into corresponding binary values.
- o The entered password is compared with a predefined password stored in the FPGA.

#### > Password Comparison:

- Combinatorial logic in the FPGA compares the entered password with the predefined password.
- o If the entered password matches the predefined password, the system sets a latch signal to indicate a correct password.

#### Alarm Activation:

- The latch signal controls the activation of the alarm and buzzer.
- If the latch signal is set (indicating an incorrect password), the alarm and buzzer are activated to signal a security breach.



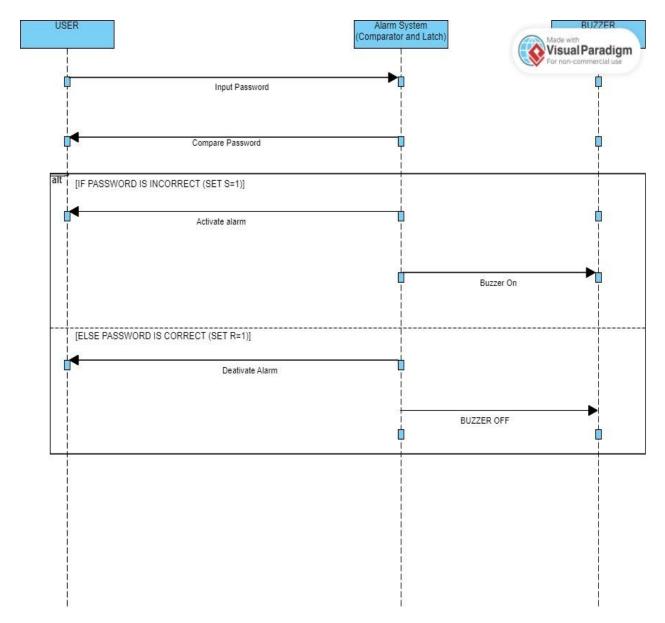


Figure 4 Sequence of system

Depiction of how our system is intended to function the states and transitions are made clear in the above sequence diagram.

## **Considerations:**

- Hardware Design:
  - Design the circuitry to interface the 4x4 matrix keypad with the Artix A7 FPGA.
  - Connect the alarm and buzzer output to appropriate pins on the FPGA board.
  - Ensure proper power supply requirements for the system.

#### > FPGA Programming:

- Write VHDL code to implement the keypad scanning algorithm, password comparison logic, and latch control.
- Simulate and verify the functionality of the code using FPGA simulation tools.

#### PCB Design:

- Design a PCB layout that incorporates the FPGA board, keypad, display (if used), and other required components.
- Ensure proper signal routing and component placement for efficient and reliable operation.

#### > Testing and Integration:

- Thoroughly test the complete system to verify its functionality and performance using test benches
- Debug any issues and make necessary adjustments to ensure proper operation.

## **Conclusion:**

The Alarm System with Password Entry provides a reliable security solution by leveraging an Artix A7 FPGA and a 4x4 matrix keypad. The system offers password-based access control and triggers an alarm in case of unauthorized attempts. By implementing the proposed design, we can ensure robust security and peace of mind.

Note: This concept proposal provides an outline for the project and can be further developed to include additional details and specifications based on project requirements.